

# Year 6 Electricity KNOWLEDGE ORGANISER



## ESSENTIAL ELECTRICITY VOCABULARY

<b>electricity</b>	The flow of electric current through a material
<b>cell</b>	A device (e.g. a battery) used to generate electricity
<b>switch</b>	A device for making or breaking the connection in an electric circuit
<b>wire</b>	A conductor that carries an electrical current through a circuit
<b>motor</b>	A device that moves when an electrical current is run to it
<b>ammeter</b>	An instrument for measuring electrical currents in amperes
<b>voltmeter</b>	An instrument for measuring electrical currents in volts
<b>conductor</b>	A material that conducts or transmits heat, electricity or sound
<b>insulator</b>	A material that does not conduct or transmit heat, electricity or sound
<b>voltage</b>	A force expressed in volts
<b>circuit</b>	An electrical device that provides a path for electrical current to flow
<b>lamp</b>	A device for giving light, often consisting of an electric bulb and its holder
<b>materials</b>	The matter something is made from
<b>insulate</b>	Protect something by preventing heat, electricity or sound from travelling
<b>symbol</b>	A mark that represents something else.

### Parallel and Series Circuits

A series circuit only has one route for the current to take. When more buzzers or bulbs are added, they share the electricity. If any parts of the series circuit is broken, the flow of current stops.

A parallel circuit has more than one route for the current to take. If one component fails the other components continue to work.




### Conductors and Insulators

A conductor is a material that allows electricity to flow through it. Some examples of electrical conductors are silver, gold, copper, steel and sea water.

An insulator is a material that does not allow electricity to flow through it. Some examples of electrical insulators are rubber, glass, oil, diamond and dry wood.
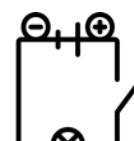
### Circuit diagrams

When drawing circuit diagrams, the wires are always drawn using straight lines. Both of these diagrams show a series circuit, but the bottom one shows the diagram using symbols.



**Mains electricity is very dangerous. We need take care when near pylons and substations.**

### Different types of electric current



**Battery electricity:** chemicals stored in batteries produce an electric current.

**Mains electricity:** electric charges are sent from power stations through wires to transformers. After that, wires carry the electricity into houses through underground wires.
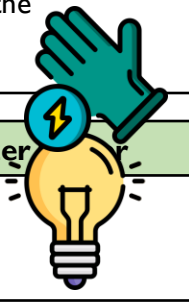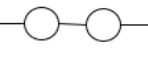
### Switches

In circuits, switches can either be open or closed. If a switch is open, the circuit is broken and electricity cannot travel through it.

If a switch is closed, the circuit is complete and electricity can travel through it. Buzzers, motors and bulbs will only turn on when the switches are closed.



### How to make a bulb brighter or a buzzer louder

- Add more batteries or a higher voltage
- Use shorter wires
- Remove any other buzzers or bulbs

### How to make a bulb dimmer or a buzzer quieter

- Use fewer batteries or a lower voltage
- Use longer wires
- Add more buzzers or bulbs to share the power

### MAKING LINKS TO PREVIOUS LEARNING GOLDEN VOCABULARY

<b>Lighthouses</b>	Lighthouses have large <b>lamps</b> which provide light to guide ships
<b>Materials</b>	Some <b>materials</b> conduct electricity and others don't.
<b>Arctic and Antarctic</b>	Animals that live in the polar regions have adapted to be <b>insulated</b>
<b>World religions</b>	Each religion has special <b>symbols</b> representing different things.

### Symbols

lamp/ bulb (indicator)	lamp/ bulb (lighting)	motor
buzzer	switch (open)	switch (closed)
cell	battery	wire